
Problem no. 4

**Design a CMOS gate circuit
for the Boolean expression
(circuits and input-
output curves)**

$$\mathbf{F = X Y + Y Z}$$

(where X, Y and Z are inputs)



Orcad Capture - [/ - (SCHEMATIC1 : PAGE1)]

File Edit View Place Macro PSpice Accessories Options Window Help

0

SCHEMATIC1-Problem 2

V1 = 10
V2 = 0
TD = 0.01m
TR = 0.01m
TF = 0.01m
PW = 10m
PER = 20m

V1 = 10
V2 = 0
TD = 0.01m
TR = 0.01m
TF = 0.01m
PW = 20m
PER = 40m

V1 = 10
V2 = 0
TD = 0.01m
TR = 0.01m
TF = 0.01m
PW = 40m
PER = 80m

V5

5

0

Simulation Settings - Problem 2

General Analysis Include Files Libraries Stimulus Options Data Collection Probe Window

Analysis type:

Time Domain (Transient)

Run to time:

80m

seconds (TSTOP)

Start saving data after:

0

seconds

Options:

☒ General Settings

☐ Monte Carlo/Worst Case

☐ Parametric Sweep

☐ Temperature (Sweep)

☐ Save Bias Point

☐ Load Bias Point

Transient options:

Maximum step size:

0.01

seconds

☐ Skip the initial transient bias point calculation (SKIPBP)

Output File Options...

OK Cancel Apply Help

ENG INTL 00:38 08/02/2024

