

## SET 1

1. Input and output voltage waveform of a full wave rectifier circuit is shown below. Design the circuit with diode D1N4001 and regenerate the following waveforms.







