

## **Problem No. – 09**

**Problem Name:** Design a Wide Bandpass filter by cascading a - 40dB/decade Low-pass Filter with a 40dB/decade High-Pass Filter

**Calculation:** l =Low pass , h =highpass

Given,

$$F(l) = 450\text{Hz}$$

$$F(h) = 3500\text{Hz}$$

Let,

$$C(l) = 0.1\mu\text{F}$$

$$C(h) = 0.01\mu\text{F}$$

From the equation we get,

$$R(l) = 321.5\Omega$$

$$R(h) = 50\text{k}\Omega$$



