

Problem No. 3

Name: Draw the input, output and transfer characteristics of CE BJT configuration according to the student ID of your group members. Also determine the value of CE current gain at a particular value.

BJT model = Q2N1566 ; 4 ≤ A ≤ 5 (A = 4)

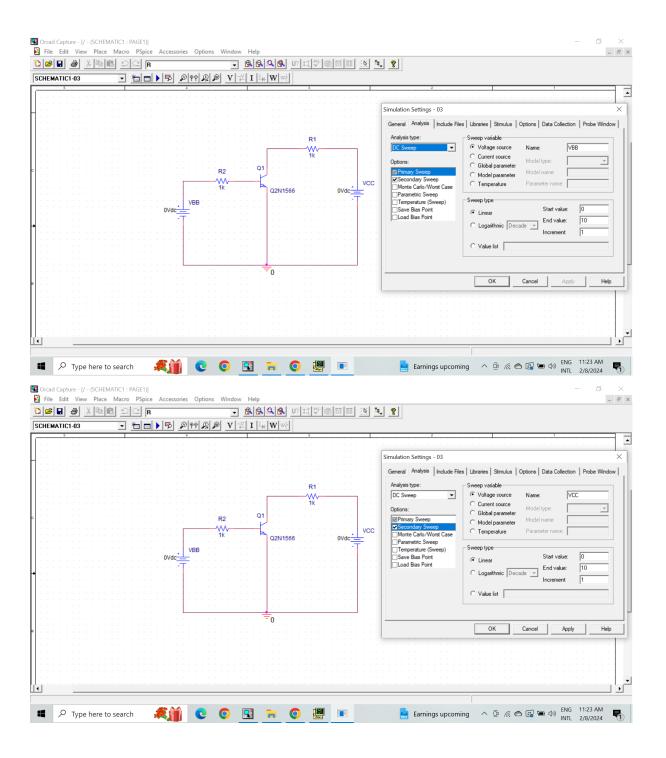

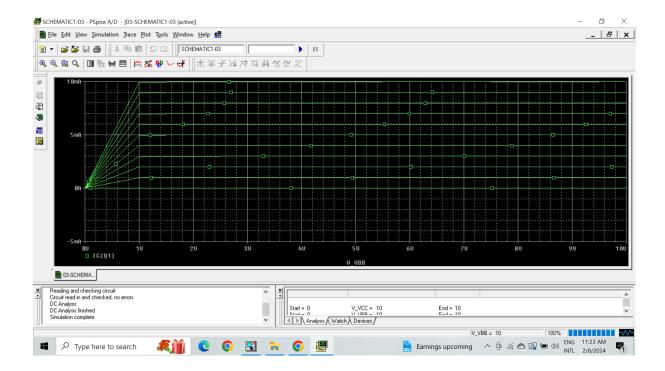

And

